
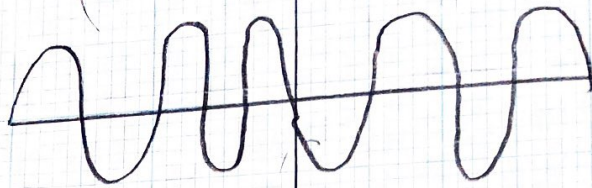


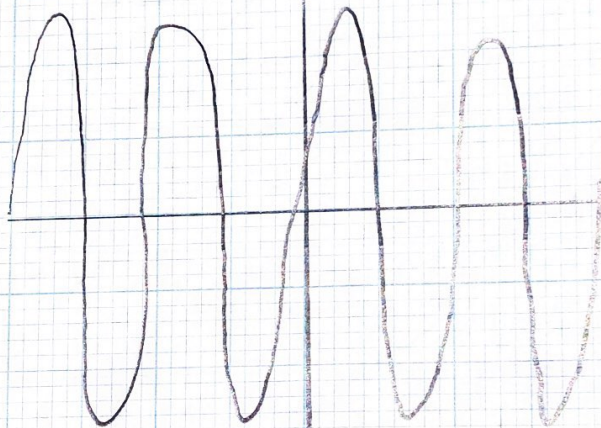
voltage across C_1
 (waveform)
 time/div = 0.5 ms
 volt/div = 5V
 (1 kHz)



note: voltage across
~~resistor~~
~~capacitor~~ = current
~~across~~ capacitor



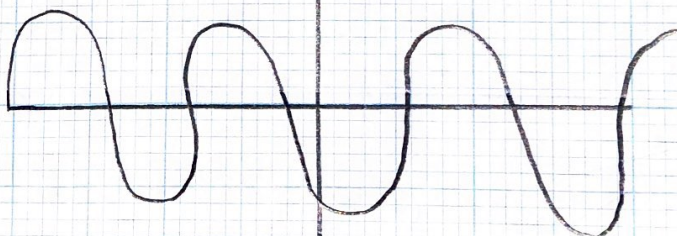voltage across R_1
 (waveform)
 time/div = 0.5 ms
 volt/div = 20 mV




voltage across
 the inductor
 at 100 Hz
 F.

measuring voltage at R_L and C_L and current

Frequency	V_C	V_R	I_C
1KHz	7.54V	0.45V	4.5×10^{-3}
2KHz	7.50V	0.91V	9.1×10^{-3}
3KHz	7.48V	1.221V	0.124
4KHz	7.25V	1.676V	0.1676
5KHz	7.03V	1.978V	0.1978
6KHz	6.93V	2.294V	0.294
7KHz	6.79V	2.586V	0.2586
8KHz	6.21V	2.893V	0.2873
9KHz	5.93V	3.014	0.3014
10KHz	5.66V	3.328	0.3328
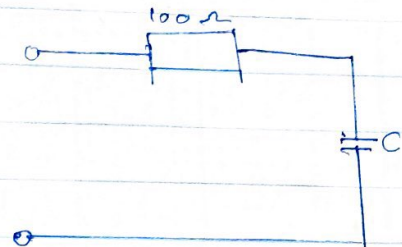
$$I_C = \frac{V_R}{R} = \frac{V_R}{100}$$



we have used an oscilloscope to draw waveforms

②

then we replaced the ~~capacitor~~ resistor with the inductor and the capacitor with resistor

F	V_L	V_R
1K	0.023V	4.986V
2K	0.035V	4.984V
3K	0.043V	4.962V
4K	0.049V	4.959V
5K	0.07V	4.957V
6K	0.075V	4.956V
7K	0.076V	4.958V
8K	0.079V	4.961
9K	0.080V	4.964 4.964
10K	0.086V	4.967
100K	0.02	

$$R = 1k\Omega$$

Log	Frequency	VC	VR
10 ^{2.1}	125.8	7.524	0.658
10 ^{2.2}	158.48	7.532	0.068
10 ^{2.3}	199.52	7.537	0.089
10 ^{2.4}	251.188	7.539	0.103
10 ^{2.5}	316.22	7.539	0.130
10 ^{2.6}	398.101	7.542	0.159
10 ^{2.7}	501.187	7.545	0.208
10 ^{2.8}	630.95	7.547	0.258
10 ^{2.9}	794.3	7.549	0.333
10 ^{3.0}	1000	7.51	0.429
10 ^{3.1}	1258.9	7.53	0.689
10 ^{3.2}	1584.8	7.52	0.861
10 ^{3.3}	1995.2	7.50	1.043
10 ^{3.4}	2511.8	7.51	1.286
10 ^{3.5}	3162.2	7.49	1.294

$$10k\Omega$$

Log	Frequency	VC	VR
	125.8	7.48	0.978
	158	7.47	0.724
	199	7.46	0.911
	251	7.44	1.026
	316	7.40	1.363
	398	7.33	1.688
	501	7.24	2.081
	630	7.06	2.587
	794	6.88	3.164
	1000	5.92	4.588
	1258.9	5.46	5.192
	1584	4.8	5.730
	2511	4.27	6.19
	3162	3.51	6.53
		3.51	6.78

④

F	V_C	V_R	V_I
1	0.016	0.009	0.017
10	0.053	0.008	0.43
20	0.053	0.008	0.35
30	0.057	0.008	0.17
40	0.058	0.007	0.046
50	0.055	0.007	0.107
60	0.051	0.007	0.198
70	0.49	0.006	0.293
80	0.048	0.007	0.468
90	0.048	0.008	0.708
100	0.045	0.007	1.030

5a) $R=100\Omega$ $L=20\mu H$ $C=0.01\mu F$

Frequency	V_{in}	V_{out}	Gain
1	2.79	0.01	
10	2.87	0.02	
20	2.90	0.02	
30	2.92	0.03	
40	2.93	0.03	
50	2.96	0.04	
60	2.99	0.06	
70	2.98	0.07	
80	2.97	0.14	
90	2.98	0.23	
100	2.99	0.09	

5b) $R = 100 \Omega$ $L = 25 \text{ mH}$ $C = 0.04 \mu\text{F}$

Frequency	$V_{in} (V)$	$V_{out} (V)$	Gain $\frac{V_o}{V_i}$
1	5.472	5.308	0.969
10	4.037	6.672	1.653
20	5.499	2.722	0.495
30	5.526	2.83	0.512
40	5.544	2.900	0.522
50	5.590	2.991	0.533
60	5.569	3.067	0.549
70	5.564	3.111	0.557
80	5.555	3.268	0.589
90	5.541	2.299	0.415
100	5.520	3.299	0.598

5c) $R = R_2 = 2100 \Omega$ $C_1 = C_2 = 0.01 \mu\text{F}$

Frequency	V_{in}	V_{out}	Gain
100	2.928	2.9	
1k	2.927	2.9	
2k	2.925	2.9	
3k	2.927	2.9	
4k	2.925	2.87	
5k	2.926	2.85	
6k	2.927	2.88	
7k	2.99	2.84	
8k	2.89	2.83	
9k	2.88	2.82	
10k	2.87	2.8	

1000 Hz $R_2 = 100 \Omega$ $C = 0.01 \mu F$

frequency	V_{in}	V_{out}	gain
100	2.927	2.91	
111	2.928	2.92	
211	2.926	2.9	
311	2.925	2.91	
411	2.929	2.9	
511	2.931	2.89	
611	2.927	2.89	
711	2.880	2.86	
811	2.931	2.83	
911	2.932	2.84	
1011	2.931	2.84	

Kalseng

09-03-2018

1000 Hz $R_2 = 100 \Omega$

$C = 0.01 \mu F$

Frequency	V_{in}	V_{out}	Gain
100	2.927	2.91	
1k	2.928	2.92	
2k	2.926	2.9	
3k	2.925	2.91	
4k	2.929	2.9	
5k	2.931	2.89	
6k	2.927	2.89	
7k	2.930	2.86	
8k	2.931	2.83	
9k	2.932	2.84	
10k	2.931	2.84	

Chalseng

09-03-2018